





12



Worksheet 8
EEL 4705
Emerging Logic Devices – AND/OR Mapping

Group #:


UIDs:

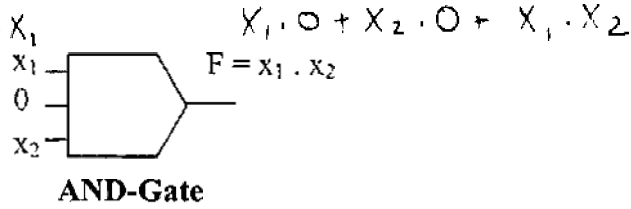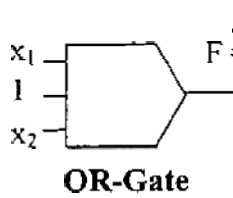

Question: Convert the following Boolean Logic expressions into equivalent Majority Gate Logic by using AND/OR mapping method demonstrated previously making use of the AND and OR forms as indicated above.

Use the method to first perform a direct AND/OR mapping of the expression. Then see if the expression can be further reduced to a simpler logic form and perform an AND OR mapping of the reduced expression.

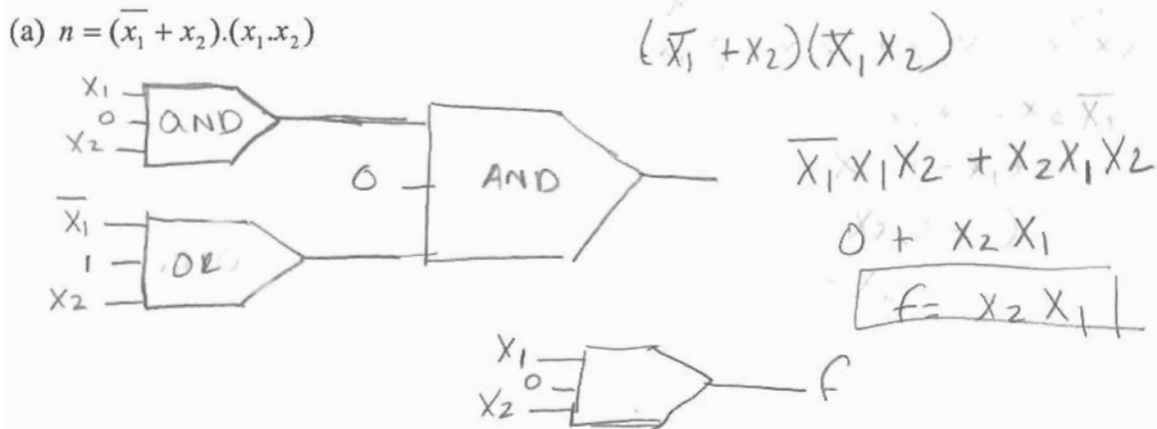Example: $n = x_1 \cdot \overline{x_2} + \overline{x_2} \cdot x_3$ can be further reduced to $n = (x_1 + x_3) \cdot \overline{x_2}$. Similarly, for all the equations below perform the AND/OR mapping for the original expression and the reduced form of the expression.



(b) $n = \overline{x_1 \cdot x_3} + \overline{x_2 \cdot x_3}$

